



Fixed-phase mesochronous CDC

Eduardo M.

cdc_tx (downlink)


- Requirements:

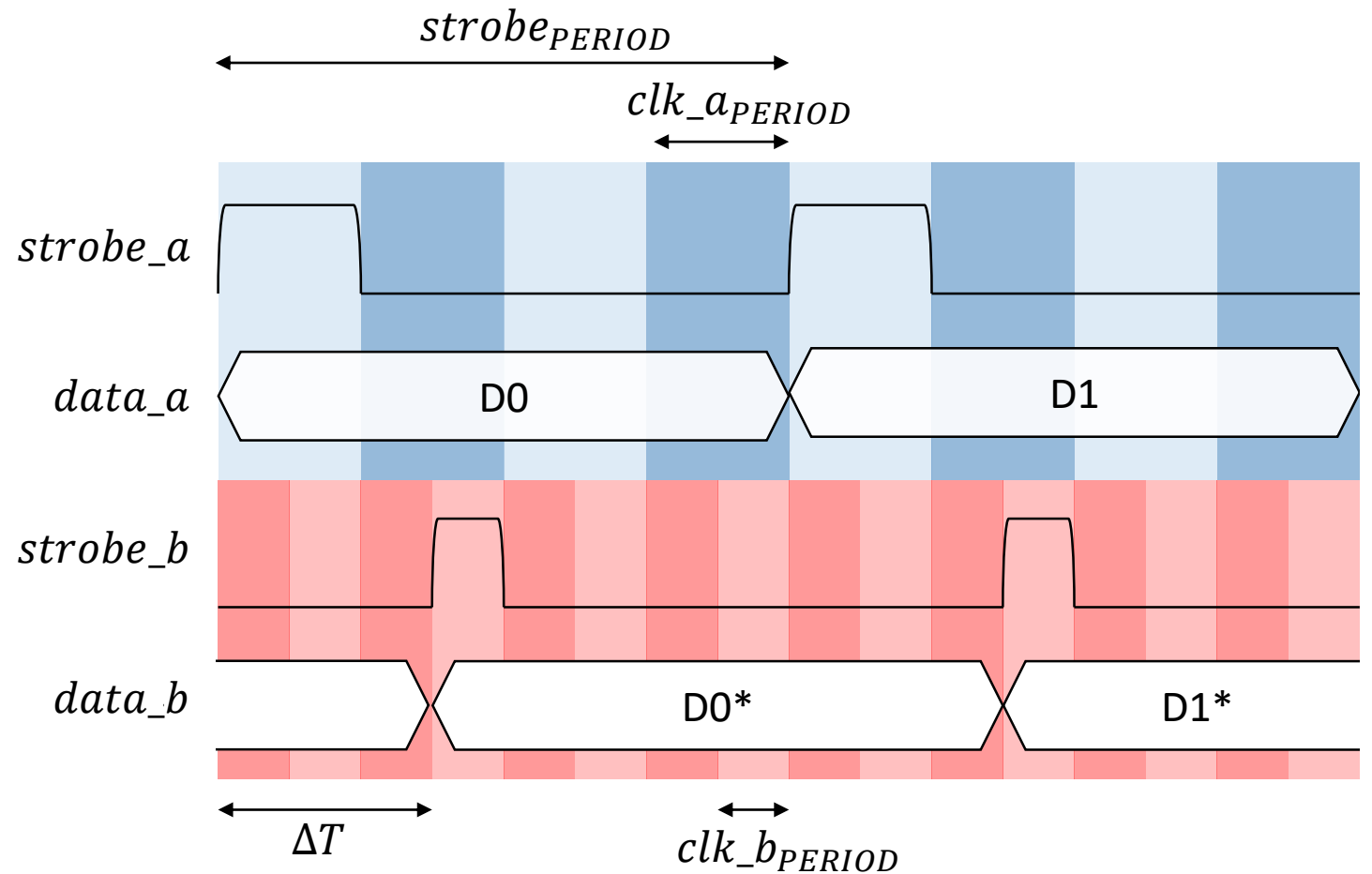 - (1) $D_n = D_n^*$ ($n=0,1,2,3,\dots$)
- (2) ΔT does not change with resets




cdc_tx (downlink)

 - Requirements:
 - (1) $D_n = D_n^*$ ($n=0,1,2,3,\dots$)





cdc_tx (downlink)

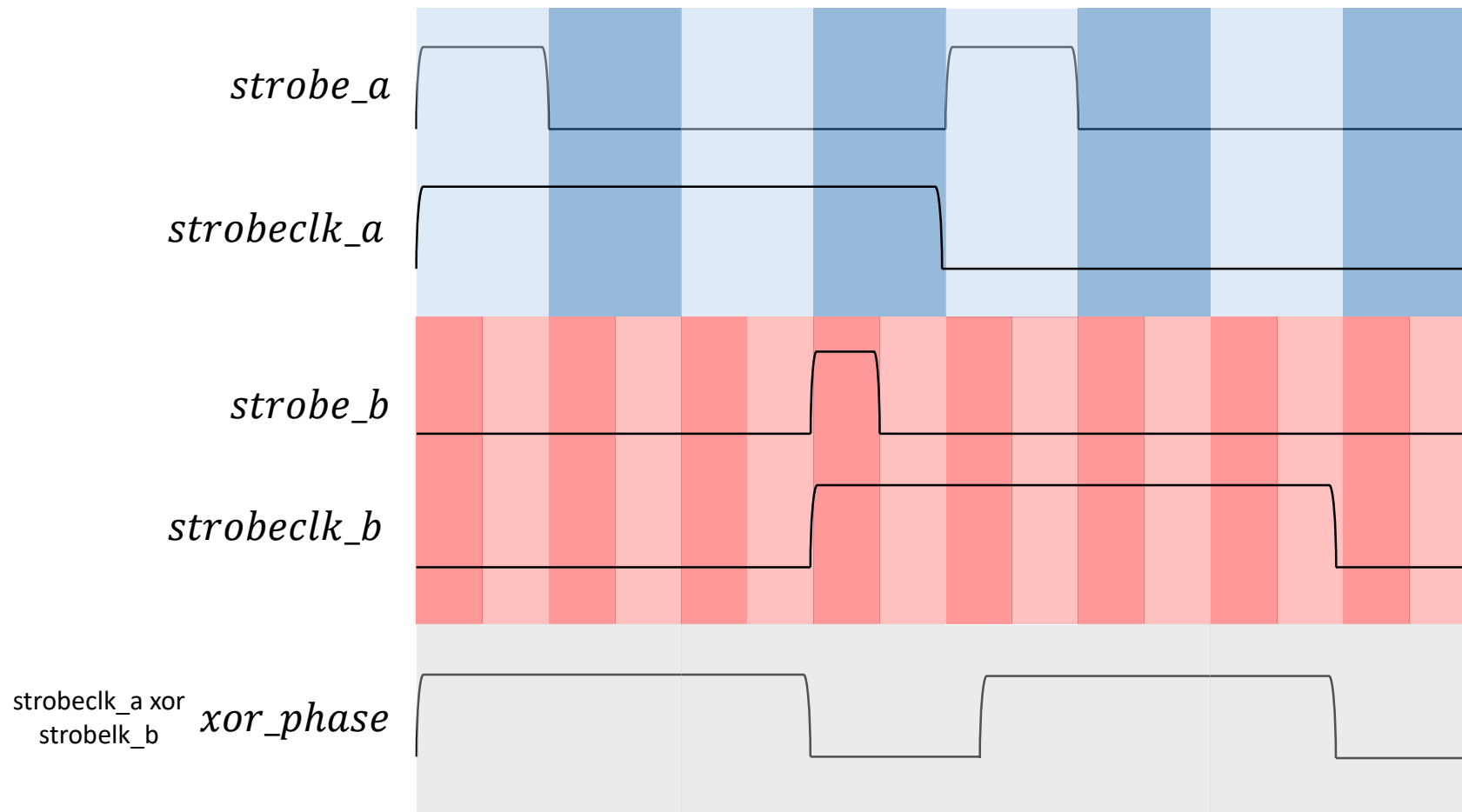- Requirements:
 - (2) ΔT does not changes with resets: measure phase between strobe_a - strobe_b



cdc_tx (downlink)

  - Requirements:
 - (2) ΔT does not change with resets: measure phase between strobe_a - strobe_b
 - Sampling xor_phase and accumulating xor with an asynchronous clock leads to a phase measurement (0-N)



ALGORITHM

- Capture phase for first reset: phase0
- For further resets:
 - If $\text{phase} > \text{phase0} + \text{clk_b_period}/2$
 - Retard strobe
 - If $\text{phase} < \text{phase0} - \text{clk_b_period}/2$
 - Advance strobe

cdc_tx (downlink)

- Summary

- This technique ensures reliable data-transfer (appropriate max_delay constraint is recommended)
- It does not require fine phase-shifting capability which is very inconvenient for designs featuring hundreds of links in a single FPGA
- It can ensure fixed-phase operation ('memory' required)
- Extensively verified in simulation for different cases

cdc_rx (uplink)

- Slightly different scheme (simplified) supporting also fixed-phase operation
 - Why different?
 - `strobe_b` is an input (fixed to 1 for 40MHz)

